



Technical Education, Vocational and Entrepreneurship
Training Authority (TEVETA)

DIPLOMA IN SCIENCE LABORATORY TECHNOLOGY

YEAR II

Physics Techniques II

Record of Practical Assessment

Learner`s Name:_____

Learner`s NRC no.:_____

Learner`s TEVETA No.:_____

Assessment Period:_____

Copyright

PREFACE

The Technical Education, Vocational and Entrepreneurship Training Authority (TEVETA) is an institution created under the Technical Education, Vocational and Entrepreneurship Training Act Number 13 of 1998, as amended by the Technical Education, Vocational and Entrepreneurship Training (Amendment) Act Number 11 of 2005.

The Act among other things provides that TEVETA shall:

- (a) regulate and conduct national examinations and assessments relating to technical education, vocational and entrepreneurship training;
- (b) charge and collect fees in respect of examinations, assessments and other services provided by the Authority;
- (c) award certificates to persons who succeed in examinations and assessments undertaken under this Act
- (d) do all such things connected with or incidental to the functions of the Authority under this Act.

Through this mandate, the Assessment and Qualifications Division of TEVETA has developed Practical Assessment Tool Kits to enable learners achieve the competences that are congruent with the demand of the workplace tasks. These tool kits in part are also intended to ensure that similar conditions under which all students in TEVET are assessed and examined apply wherever the course is undertaken in Zambia.

The Trainers shall work with the Learners to collect evidence of competence, using the benchmarks provided by the unit standards. During the year, the Learners shall be required to undertake a series of practical assessment tasks. It is the sum of all these assessments tasks that deems a Learner to be competent (or not).

This approach to assessment is not a one-off event but one that gives learners many opportunities to demonstrate skill and allow for the capturing and recording of these demonstrations.

For the Learner to be deemed competent, they must demonstrate competency in every aspect of the practical tasks being undertaken. It must however be understood by the Trainer that Competency does not mean expert. It means that the candidate has attained sufficient skill and knowledge to perform the activity or service to a degree and quality that is acceptable to the industry and the customer in a time within which a competent person at the level could reasonably be expected to perform the task.

While this will be undertaken at institutional level, it is therefore envisaged that the Assessment principles of VALIDITY, RELIABILITY, FAIRENESS and FLEXIBILITY shall at all times be adhered to.



Pre-Assessment

Assessment process explained to the employee (✓ if Yes).	<input type="checkbox"/>
Any appeal relating to the outcome of the assessment or the way in which the assessment was conducted shall be made through the company's <i><u>fair treatment policy</u></i> as explained to the employee (✓ if Yes).	<input type="checkbox"/>

Employee/Trainee Employee/Trainee name: _____ (Print) Employee/Trainee comments:	Assessor Assessor name: _____ (Print) Assessor comments:	
I fully understand the assessment and appeals process.	Theory assessment sighted and checked as satisfactory.	<input type="checkbox"/>
Signature: _____ Date: _____	Signature: _____ Date: _____	

Table of Contents

Page

Technical Education, Vocational and Entrepreneurship Training Authority (TEVETA)

(unit code) 671 Physics Techniques

Record of Practical Assessment	1
Preface	2
Pre-assessment	3
Table of Contents	4
Prepare for practical assessment	5
Work health and safety	5
Customising the assessment	5
Carrying out the assessment	5
Completing the assessment	5
Assessor qualifications	5
Expiry status of assessment	5
Resources required	5
Range of variables	5
1. Dependence of resistance on length and cross sectional area.	6
2. Charging and discharging of a capacitor	8
3. Determining the temperature dependence of resistance.	9
4. Determination of capacitive reactance in RC-circuit	10
5. Determination of inductive reactance in RL-Circuit	11
6. Determining waveforms of rectification circuits	12
7. Determination of transistor Switching voltage	13
8. RC coupled transistor amplifier	14
9. Operational amplifier as inverting amplifier	15
10. Operational amplifier as differential amplifier	16
11. Final Assessment Summary	17
12. Assessment Outcome	19
13. Validation of the assessment	20



Prepare for the practical assessment

Add text here

Work Health and Safety

Add text here

Customising the assessment

Add text here

Carrying out the assessment

Add text here

Completing the assessment

Add text here

Assessor qualifications

Add text here

Expiry status of assessment

Add text here

Resources required

Add text here

Range of variables

Add text here

Observation Checklist

1. DEPENDANCE OF RESISTANCE ON LENGTH AND CROSS SECTIONAL AREA	Satisfactory			Not Satisfactory		
During observation of work activities, the candidate demonstrated that they can:	Attempt No			Attempt No		
	1	2	3	1	2	3
<p>a) Determining the dependence of Resistance on length of conductor. This includes</p> <ul style="list-style-type: none"> <input type="checkbox"/> Setting up circuit correctly with 1m Nichrome wire and Ameter in series with another fixed resistor. <input type="checkbox"/> Connecting a voltmeter to a jokey and fix at one end of Nichrome wire. <input type="checkbox"/> Make the jokey have contact with the wire at four (4) different points. <input type="checkbox"/> Each time a contact is made, measure and record voltage, current and length. <input type="checkbox"/> Calculating values of resistance. <input type="checkbox"/> Drawing graph of Resistance against Length <input type="checkbox"/> Stating the mathematical relationship between Resistance and Length. 						
<p>b) Determining the dependence of Resistance on Cross-sectional area. This includes</p> <ul style="list-style-type: none"> <input type="checkbox"/> Connecting circuit correctly with Nichrome wire in series with a fixed resistor. <input type="checkbox"/> Connecting the voltmeter across the nichrome wire. <input type="checkbox"/> Switching on circuit and measure voltage, current and diameter of Nichrome wire. <input type="checkbox"/> Replace with another Nichrome wire of different and measure voltage, current and diameter. <input type="checkbox"/> At least four wires of different diameters shall be used. <input type="checkbox"/> Calculating the values of Resistance and values of $\frac{1}{Area}$. <input type="checkbox"/> Plotting a graph of Resistance against $\frac{1}{Area}$ <input type="checkbox"/> Stating the mathematical equation that Connects Resistance and Area. <input type="checkbox"/> Combine the two equations and Determining the value of this constant in the combined equation with its units. 	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>



Assessor comments:

Signed: Assessor:

Trainee:

2. CHARGING AND DISCHARGING OF A CAPACITOR	Satisfactory			Not Satisfactory		
During observation of work activities, the candidate demonstrated that they can:	Attempt No			Attempt No		
	1	2	2	1	2	3
a) Verify the time constant of a capacitor by considering its discharge curve. This includes <ul style="list-style-type: none"> <input type="checkbox"/> Setting up circuit correctly with the power supply charging the capacitor through a low value resistor. <input type="checkbox"/> When the first ammeter reading is low and constant, flip Switching to second circuit and take current reading of second ammeter every five second. <input type="checkbox"/> Plotting a graph of Current against time. <input type="checkbox"/> Calculating the gradient. <input type="checkbox"/> By comparing with discharge equation find the time constant and its percentage error 	<input type="checkbox"/>			<input type="checkbox"/>		

Assessor comments:

Signed: Assessor:

Trainee:



3. DETERMINING THE TEMPERATURE DEPENDANCE OF RESISTANCE.	Satisfactory			Not Satisfactory		
During observation of work activities, the candidate demonstrated that they can:	Attempt No			Attempt No		
	1	2	2	1	2	3
a) Determining the relationship between resistance and temperature of a resistor. This includes <ul style="list-style-type: none"> <input type="checkbox"/> Setting up circuit correctly with the resistor properly placed in a watery bath. <input type="checkbox"/> Setting the water bath temperature and record the temperature, voltage and current. <input type="checkbox"/> Adjust waterbath temperature and when it stabilizes, record temperature, voltage and current. <input type="checkbox"/> Repeat the temperature adjustment and recording until five (5) Settings of data are available and spread over a wide range of temperature. <input type="checkbox"/> Plotting a graph of Resistance against Temperature. <input type="checkbox"/> From graph Determining gradient and vertical intercept. <input type="checkbox"/> By comparison with Resistance – temperature equation, obtain values of R_0 and α. 	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Assessor comments:

Signed: Assessor:

Trainee:

4. DETERMINATION OF CAPACITIVE REACTANCE IN RC-CIRCUIT	Satisfactory			Not Satisfactory		
During observation of work activities, the candidate demonstrated that they can:	Attempt No			Attempt No		
	1	2	2	1	2	3
a) Determining the Capacitive Reactance in RC circuit. This includes <ul style="list-style-type: none"> <input type="checkbox"/> Setting up circuit correctly with ac voltmeter and ac ammeters correctly. <input type="checkbox"/> Setting the functional generator to 50Hz and measure source voltage, capacitor voltage and current correctly. <input type="checkbox"/> Repeat with frequency increase of 100Hz or more correctly. <input type="checkbox"/> Calculating values of Circuit resistance and $\frac{1}{\text{frequency}}$ correctly. <input type="checkbox"/> Determining the gradient and vertical intercept correctly. <input type="checkbox"/> By comparing with impedance equation, Calculating the values of Capacitance and fixed resistor correctly. <input type="checkbox"/> Calculating percentage error in your values correctly. 	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Assessor comments:

Signed: Assessor:

Trainee:



5. DETERMINATION OF INDUCTIVE REACTANCE IN RL-CIRCUIT	Satisfactory			Not Satisfactory		
During observation of work activities, the candidate demonstrated that they can:	Attempt No			Attempt No		
	1	2	2	1	2	3
a) Determining the Inductive Reactance in RL circuit. This includes <ul style="list-style-type: none"> <input type="checkbox"/> Setting up circuit correctly with ac voltmeter and ac ammeters correctly. <input type="checkbox"/> Setting the functional generator to 50Hz and measure source voltage, capacitor voltage and current correctly. <input type="checkbox"/> Repeat with frequency increase of 100Hz or more correctly. <input type="checkbox"/> Calculating values of Circuit resistance correctly. <input type="checkbox"/> Determining the gradient and vertical intercept correctly. <input type="checkbox"/> By comparing with impedance equation, Calculating the values of Inductance and fixed resistor correctly. <input type="checkbox"/> Calculating percentage error in your values correctly.. 	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Assessor comments:

Signed: Assessor:

Trainee:

6. DETERMINING WAVEFORMS OF RECTIFICATION CIRCUITS	Satisfactory			Not Satisfactory		
During observation of work activities, the candidate demonstrated that they can:	Attempt No			Attempt No		
	1	2	2	1	2	3
a) Determining the output wave of Half-wave rectifier. This includes <ul style="list-style-type: none"> <input type="checkbox"/> Connecting the circuit correctly. <input type="checkbox"/> Connecting the Dual Channel Oscilloscope to both input and output terminals of circuit correctly. <input type="checkbox"/> By adjusting the time-base and voltage Settings for both channels correctly, view both waveform on the Oscilloscope. <input type="checkbox"/> Drawing the wave forms for both input and output correctly. 						
b) Determining the output wave of Full-wave rectifier. This includes <ul style="list-style-type: none"> <input type="checkbox"/> Connecting the circuit correctly. <input type="checkbox"/> Connecting the Dual Channel Oscilloscope to both input and output terminals of circuit correctly. <input type="checkbox"/> By adjusting the time-base and voltage Settings for both channels correctly, view both waveform on the Oscilloscope. <input type="checkbox"/> Drawing the wave forms for both input and output correctly. 	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Assessor comments:

Signed: Assessor:

Trainee:



7. DETERMINATION OF TRANSISTOR SWITCHING VOLTAGE	Satisfactory			Not Satisfactory		
During observation of work activities, the candidate demonstrated that they can:	Attempt No			Attempt No		
	1	2	2	1	2	3
a) Determining experimentally the base Switching of the transistor. This includes <ul style="list-style-type: none"> <input type="checkbox"/> Connecting the circuit correctly. <input type="checkbox"/> Adjusting the variable resistor correctly. <input type="checkbox"/> Recording the base voltage at which the LED on the collector terminal comes on. <input type="checkbox"/> Suggesting circuit types that can apply the transistor as a Switching. 	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Assessor comments:

Signed: Assessor:

Trainee:

8. RC COUPLED TRANSISTOR AMPLIFIER	Satisfactory			Not Satisfactory		
During observation of work activities, the candidate demonstrated that they can:	Attempt No			Attempt No		
	1	2	2	1	2	3
a) Build an RC coupled transistor amplifier and test its operation. This includes <ul style="list-style-type: none"> <input type="checkbox"/> Connecting the circuit correctly. <input type="checkbox"/> Connecting the signal tracking cables from the Oscilloscope correctly. <input type="checkbox"/> Feeding in a signal from a Signal Generator and monitor input and output correctly. <input type="checkbox"/> Drawing both input and output signals correctly. <input type="checkbox"/> Scanning the frequency range of the amplifier correctly. 	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Assessor comments:

Signed: Assessor:

Trainee:



9. OPERATIONAL AMPLIFIER AS INVERTING AMPLIFIER	Satisfactory			Not Satisfactory		
During observation of work activities, the candidate demonstrated that they can:	Attempt No			Attempt No		
	1	2	2	1	2	3
a) Build, Test and Operate an Op-Amp based Inverting Amplifier. This includes <ul style="list-style-type: none"> <input type="checkbox"/> Drawing a correct design of Inverting Op-Amp amplifier. <input type="checkbox"/> Setting up circuit correctly with both input and output terminals tracked by oscilloscope. <input type="checkbox"/> Feeding input with signal generator correctly. <input type="checkbox"/> Drawing the input and output signals in real time correctly. <input type="checkbox"/> Stating on use of the op-amp amplifier in this mode. 	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Assessor comments:

Signed: Assessor:

Trainee:

10. OPERATIONAL AMPLIFIER AS DIFFERENTIAL AMPLIFIER	Satisfactory			Not Satisfactory		
During observation of work activities, the candidate demonstrated that they can:	Attempt No			Attempt No		
	1	2	2	1	2	3
a) Build, Test and Operate an Op-Amp based Differential Amplifier. This includes <ul style="list-style-type: none"> <input type="checkbox"/> Drawing a correct design of Differential Op-Amp amplifier. <input type="checkbox"/> Setting up circuit correctly with both input and output terminals tracked by oscilloscope. <input type="checkbox"/> Feeding input with signal generator correctly. <input type="checkbox"/> Drawing the input and output signals in real time correctly. <input type="checkbox"/> Stating on use of the op-amp amplifier in this mode. 	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>	<input type="checkbox"/>

Assessor comments:

Signed: Assessor:

Trainee:



Final Assessment Summary

Practical assessment summary

Note: refer to mapping document if required

		Satisfactory	Not Satisfactory
1.	Dependence Of Resistance On Length And Cross Sectional Area	<input type="checkbox"/>	<input type="checkbox"/>
2.	Charging And Discharging Of Discharging Of A Capacitor	<input type="checkbox"/>	<input type="checkbox"/>
3.	Determining The Temperature Dependence Of Resistance	<input type="checkbox"/>	<input type="checkbox"/>
4.	Determination Of Capacitive Reactance In RC-Circuits	<input type="checkbox"/>	<input type="checkbox"/>
5.	Determination Of Inductive Reactance In RL Circuits	<input type="checkbox"/>	<input type="checkbox"/>
6.	Determining Waveforms Of Rectification Circuits	<input type="checkbox"/>	<input type="checkbox"/>
7.	Determination Of Transistor Switching Voltage	<input type="checkbox"/>	<input type="checkbox"/>
8.	RC Coupled Transistor Amplifier	<input type="checkbox"/>	<input type="checkbox"/>
9.	Operational Amplifier As Inverting Amplifier	<input type="checkbox"/>	<input type="checkbox"/>
10.	Operational Amplifier As Differential Amplifier		

[illegible]

Satisfactory ☐

Employee/Trainee

Assessor

Employee/Trainee comments:

Assessor comments:

Signature: _____

Signature: _____

Date: _____

Date: _____

VALIDATION OF THE ASSESSMENT

NAME:..... DATE:.....

POSITION: **PRINCIPAL/HEAD OF INSTITUTION** SIGNATURE:.....

NAME INSTITUTION:.....

STAMP:

